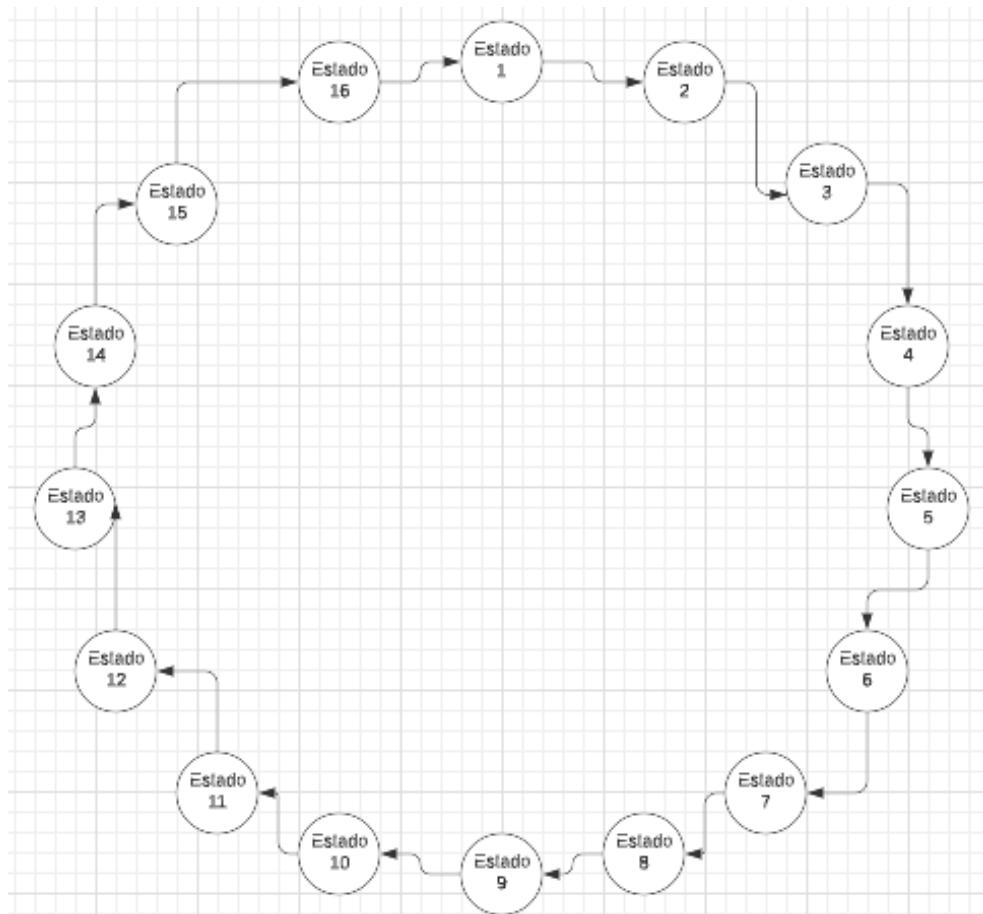


Tabela Verdade para o cruzamento 4B

Contador		S1	S2	S3	S4	S5	S6	S7	S8
0000	Estado 1	Green	Green	Red	Red	Red	Red	Red	Green
0001	Estado 2		Green	Red	Red	Red	Red	Red	Green
0010	Estado 3	Green	Green	Red	Red	Red	Red	Red	Green
0011	Estado 4	Yellow	Green	Red	Red	Red	Red	Red	Yellow
0100	Estado 5	Red	Green	Green	Green	Red	Red	Red	Red
0101	Estado 6	Red	Green	Green	Green	Red	Red	Red	Red
0110	Estado 7	Red	Green	Green	Green	Red	Red	Red	Red
0111	Estado 8	Red	Yellow	Yellow	Yellow	Red	Red	Red	Red
1000	Estado 9		Red	Red	Red	Green	Green	Red	Green
1001	Estado 10		Red	Red	Red	Green	Green	Red	Green
1010	Estado 11		Red	Red	Red	Green	Red	Red	Green
1011	Estado 12		Red	Red	Red	Yellow	Green	Red	Green
1100	Estado 13		Red	Red	Green	Red	Green	Red	Green
1101	Estado 14		Red	Red	Green	Red	Green	Red	Green
1110	Estado 15		Red	Red	Green	Red	Green	Red	Green
1111	Estado 16		Red	Red	Yellow	Red	Yellow	Yellow	Green

Máquinas de Estado para a tabela acima



Circuito

